

CSE 306 : Offline 2

Floating Point Adder Simulation

May 30, 2021

Lab Section : B2
Group 03

1705093

1705098

1705103

1705110

1705119

1 Introduction

Floating point numbers are numbers that contain floating decimal points. They are used to represent real numbers in computing. For us to perform arithmetic addition/subtraction operation on floating point numbers, we need a circuit known as a Floating Point Adder (FPA).

A Floating Point Adder performs addition/subtractions on floating point numbers in their binary representation. The IEEE-754 standard describes a standard binary format representation way of floating point numbers. The binary bits are stored as below:



2 Problem Specification

To design a floating point adder circuit which takes two signed floating point numbers as inputs and provides their sum, another floating point as output. The floating points are of 16-bits and thus be represented as follows:



3 Algorithm Flowchart

The algorithm flowchart for Floating Point Addition is shown in Figure 1

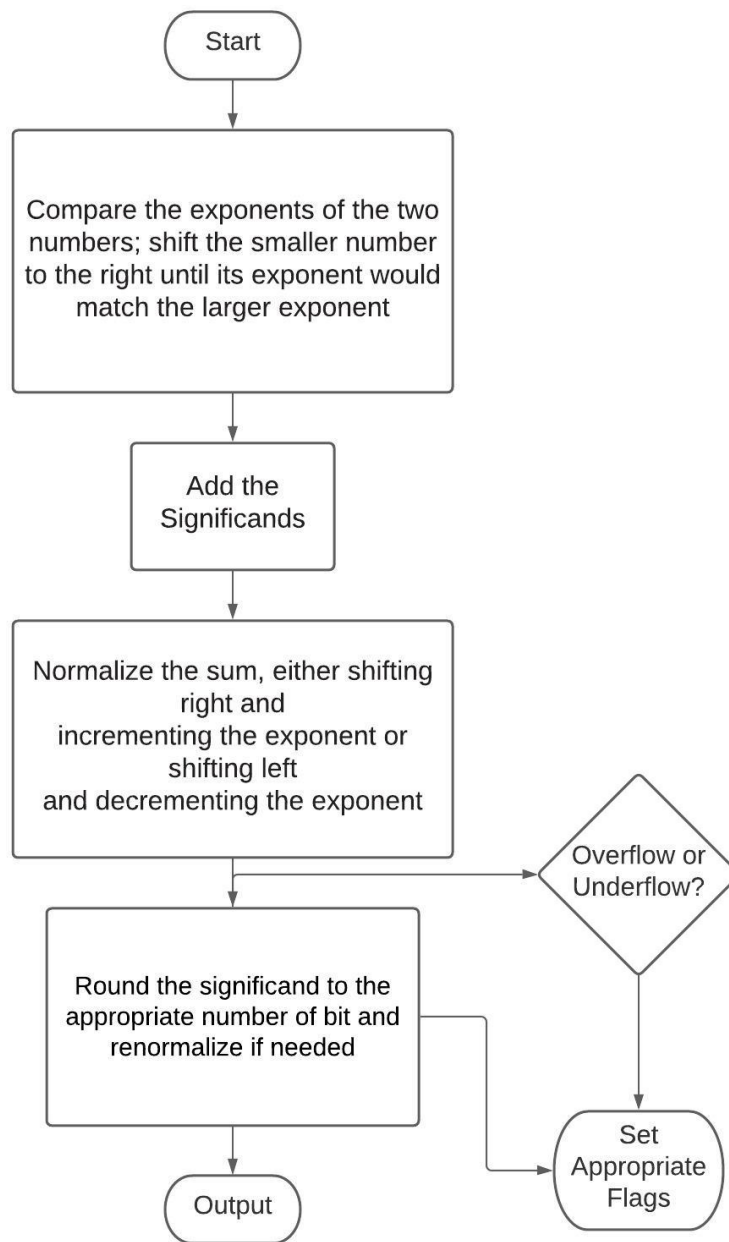


Figure 1: Floating Point Addition

4 High-Level Block Diagram

A very high-level block diagram of the floating point adder is shown in Figure 2

 


Figure 2: High-level Block Diagram of the Floating Point Adder

5 FPA Block Diagram

The detailed block diagram with all the components is shown in Figure 3

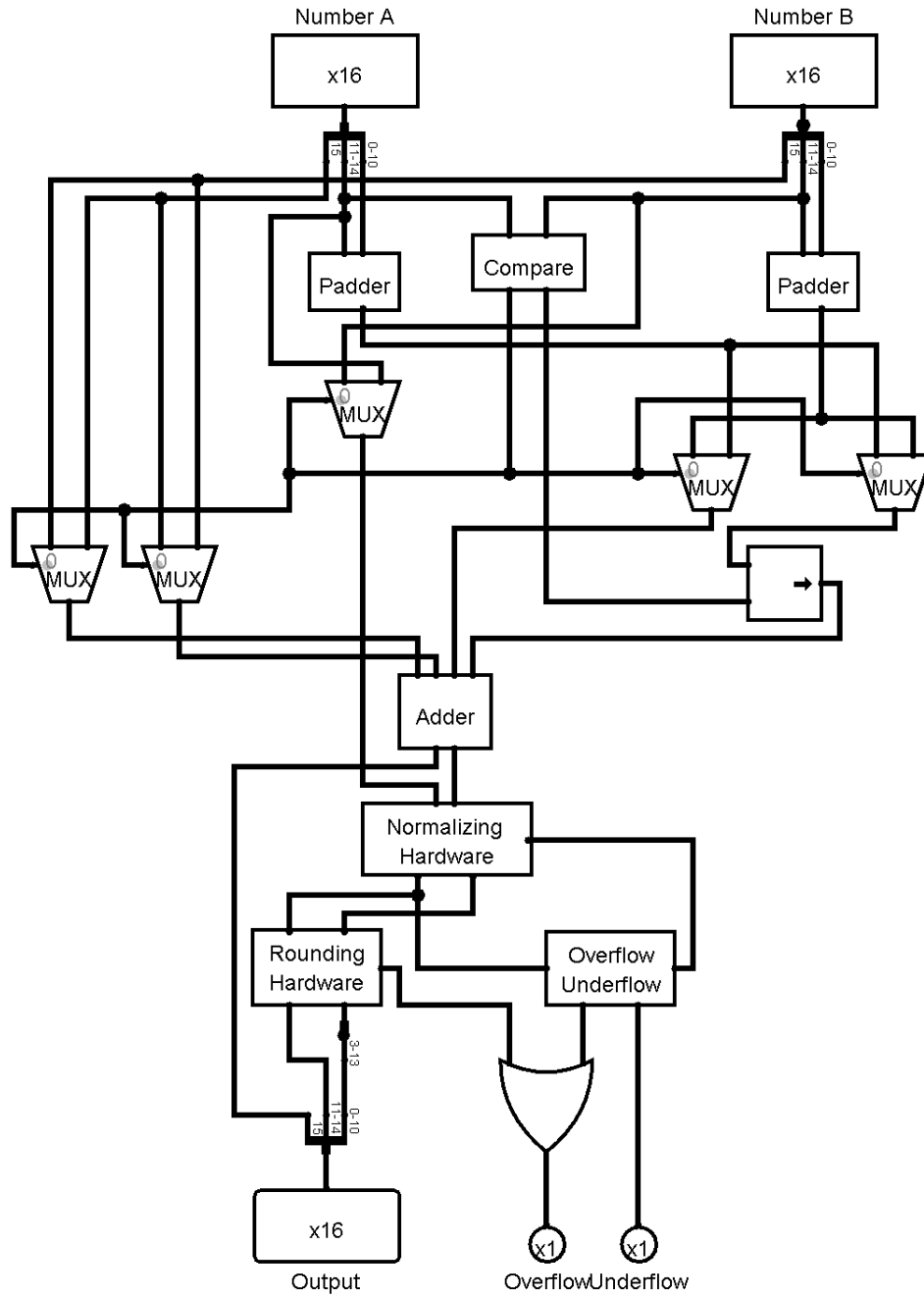


Figure 3: Block Diagram of the components inside Floating Point Adder

6 Overview of the components

6.1 Compare Block

The Compare block compares the exponents and outputs the absolute value of their difference. It contains a 4-bit subtractor whose output, $(B - A)$, is sent to a MUX both directly and in negated form. The 4-bit negator performs 2's complement on its input. If $A > B$, the borrow out is 1 and the MUX outputs the negated value of subtractor to get the absolute difference. Otherwise, if $B > A$, the direct value is output.

 


Figure 4: Circuit Diagram of the Compare Block

6.2 Padder

The padder converts the 11 bit fraction to a 16 bit significand as follows:

$$\text{Significand} = 0X \text{ } 11\text{-bitFraction} \text{ } 000$$

The 0X padded to the left represents two binary digits to the left of the binary point. Here X is 1 if the exponent is non-zero, otherwise X is 0. These two extra binary bits make the normalization hardware much simpler. The 000 padded to the right allows us to perform rounding later on. While padding with one extra bit to the right would have been enough, we store three extra bits because the IC count for both 14-bit and 16-bit adders/MUX are same when they are built by cascading 4-bit units. So the two extra bits reduce the precision lost during shifting without affecting the IC count.

6.3 Series of MUXs

We have a series of MUXs each of which use the $(\text{ExponentA} > \text{ExponentB})$ output from the Compare Block as their selection bit. These MUXs are used as follows:

- One MUX to select the larger Exponent

 


Figure 5: Circuit Diagram of the Padder Block

- One MUX to select the Significand with the larger Exponent and another MUX to select its corresponding Sign
- One MUX to select the Significand with the smaller Exponent and another MUX to select its corresponding Sign

 


Figure 6: Circuit Diagram of the Series of MUXs

6.4 Shifter

We want the exponent part of both the numbers to be the same before they are added. For this purpose the shifter is used which right-shifts the significand of the number with the smaller exponent. The shift amount is determined by the absolute value of the difference between the exponents. We are not providing any diagram showing the internal implementation of the shifter because we used the shifter circuit readily provided by Logisim.

6.5 Adder

The input to the Adder are the two Significands and their corresponding Signs.

- If any 1 is present in the Significand
- The number of positions the highest set bit needs to be shifted for the output to be in normalized form.

For Normalization left shift by 0-14 bits might be needed, or right shift by 1 bit maybe needed. To simplify the situation we used Left Rotator instead because left rotation by 15 bits is the same as right shift by 1 bit in this case.

If the amount of left shift needed is greater than or equal to the value of the exponent, then the output will be a Denormal number. The Significand is shifted Exponent-1 times to the left and the output Exponent is 0000.

If the value of the output Exponent is 1111, then it is a case of overflow. And according to IEEE-754's representation of infinity, the Fraction part of the Significand is made all 0s.

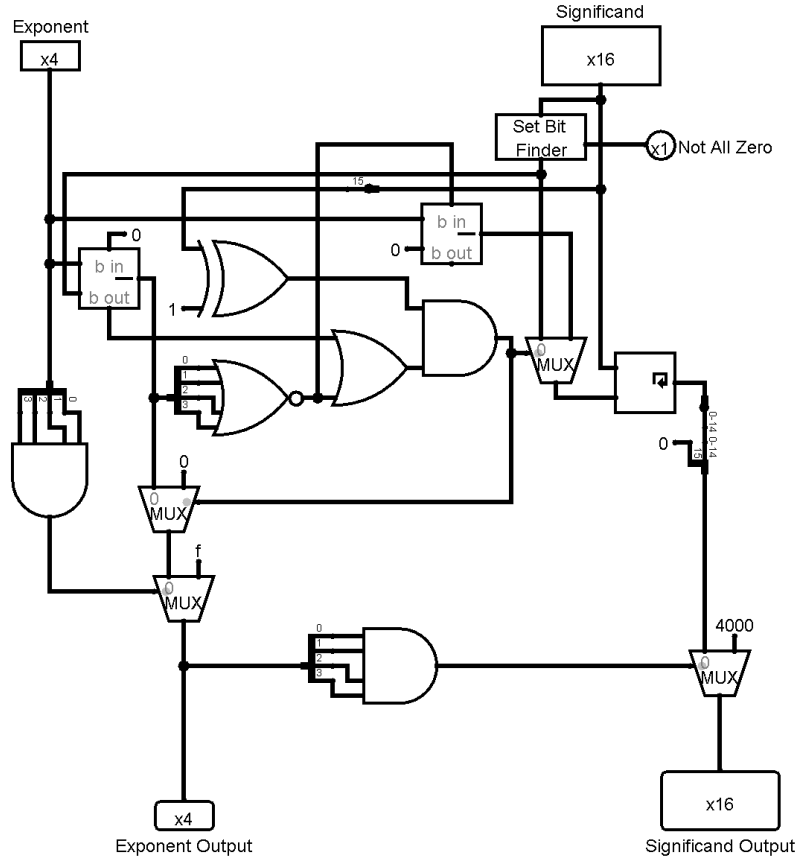


Figure 8: Circuit Diagram of the Normalization Hardware

6.7 Set Bit Finder

It takes the 16-bit Significand as input and then reverses the input. The index of the lowest set bit is found and 1 is subtracted from it. The resulting value is equal to

the number of left rotation needed for the Significand to be converted to Normalized form.

 


Figure 9: Circuit Diagram of the Set Bit Finder

6.8 Rounding Hardware

We have taken the Significand and Exponent as input and given as output the final Significand, Exponent and Overflow detection. We check the 3rd bit from right to understand if rounding is needed. If the 3rd bit from right is 1, we round the Significand by adding it to a binary number with 1 at the 4th bit from right and 0's elsewhere. If rounding causes number to become un-normalized, we right shift the Significand by 1 and add 1 to the Exponent.

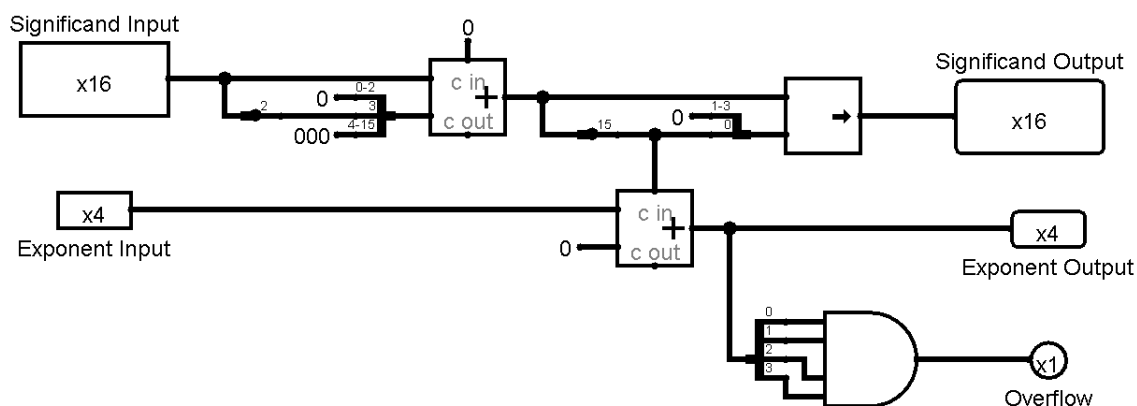


Figure 10: Circuit Diagram of the Rounding Hardware

6.9 Overflow/Underflow

Overflow occurs when all bits of the Exponent are 1. Underflow occurs when all bits of the Exponent are 0 but all bits of the Significand are not 0

 


Figure 11: Circuit Diagram of the Overflow/Underflow detector

7 IC Count

Operation	IC Number	Count
QUAD 2-AND	7408	1
DUAL 4-AND	7421	2
QUAD 2-OR	7432	1
DUAL 4-OR	744072	1
QUAD 2-XOR	7486	1
DUAL 4-NOR	7425	1
4 bit Adder	7483	9
4 bit Subtractor	-	4
16 bit Comparator	-	1
16 bit Right Shifter	-	2
16 bit Left Rotator	-	1
Set Bit Finder	-	1
Negator	-	2
Quad 2:1 MUX	74157,158	30
		Total : 57

8 Simulation Platform

Logisim-2.7.10

9 Discussion

About a week before the submission deadline the problem was simplified as follows:

- The input numbers would strictly be in Normalized form
- Truncation was allowed instead of rounding

However by that time we had already progressed significantly with our work where we had handled inputs in Normalized/Denormal/0/Infinity form. Also we had implemented rounding instead of truncation as per the original specification. So we believe the large number ICs required in our implementation is due to the additional functionality - not due to any form of inefficiency in circuit design.

We assumed that IC minimization across different components is allowed. For example: 1 XOR gate was required in the Normalization Hardware and 1 XOR gate was required in the Adder. So both of these can be implemented using the same 7486-XOR IC.

After rounding the number can become de-normalized. So it must be fed back to the Normalization Hardware. However, this means the process would involve clock pulses. To avoid the use of clock pulses we identified the specific scenario where this problem would occur and handled it separately. This means our circuit remains a combinational one, however this approach does increase IC count slightly.